

Ding Dong Doorbell

It's that classic "ding dong" sound everyone loves – but this one is electronic, of course. Why not build one for your front door?

What does it do?

This electronic doorbell simulates the sound of the electromechanical ding-dong doorbell.

The latter uses two plates which resonate when struck by a small soft hammer, one plate producing a "ding" sound and the second plate the "dong". When the doorbell switch is pressed, current flows through a solenoid which activates the hammer to strike the "ding" plate. When the doorbell switch is opened, the solenoid plunger returns by a spring and strikes the second "dong" plate.

The electronic version works in a similar manner – press the button and you get the "ding" sound, release it for the "dong".


Construction

All parts except the remote loudspeaker are mounted onto the Electronic Doorbell PC board.

Start by installing the PC stakes at all external wiring points and for the speaker, followed by the resistors and then VR1. When inserting IC1 make sure that it is oriented

with pin 1 in the position shown. Diode D1 mounts with the cathode (striped end) towards S1 and D2 with the cathode towards Q1.

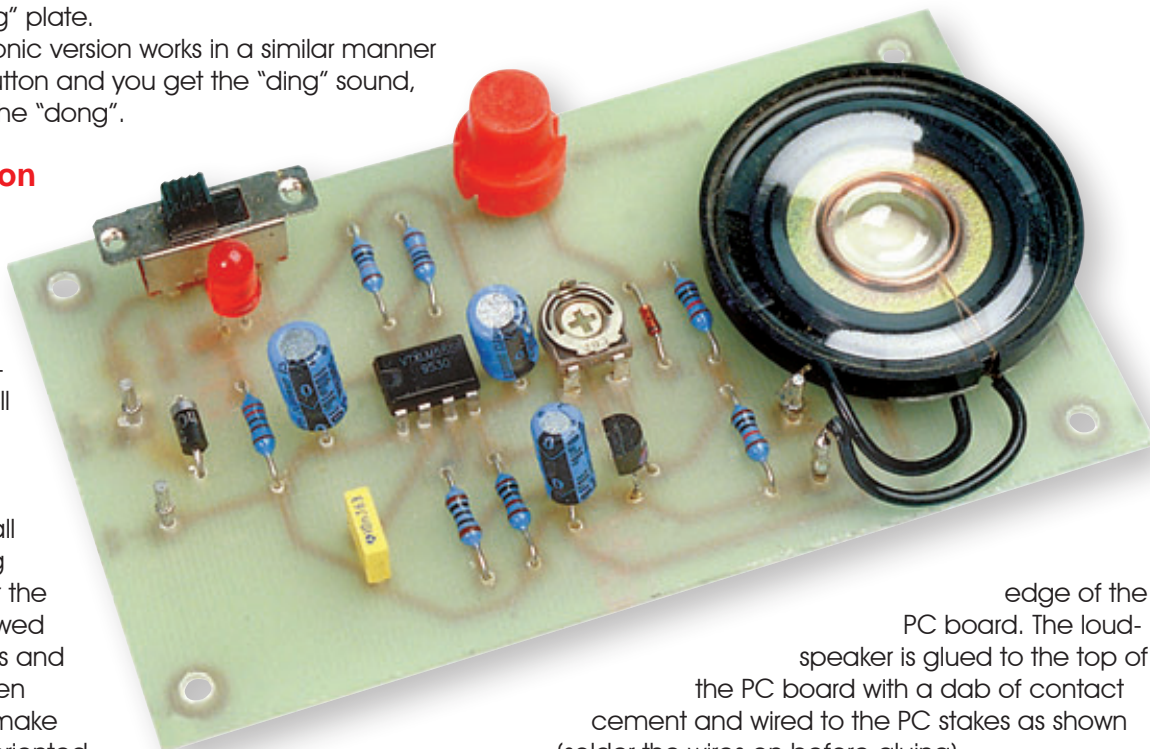Install the electrolytic capacitors, LED1 and transistor Q1 with the polarity shown. S1 is installed by inserting the switch pins into the PC board and soldering in place. Switch S1 may be a DPDT type; this doesn't matter. Switch S2 must be correctly oriented with the "flat" side of the switch body towards the



edge of the PC board. The loudspeaker is glued to the top of the PC board with a dab of contact cement and wired to the PC stakes as shown (solder the wires on before gluing).

You will need these parts

Resistors (0.25W, 1%)

2 100kΩ 2 10kΩ 1 2.2kΩ

1 1kΩ 1 100Ω

1 20kΩ horizontal trimpot (VR1)

Capacitors

1 100μF 16VW electrolytic

1 47μF 16VW electrolytic

1 10μF 16VW electrolytic

1 .01μF MKT polyester

Semiconductors

1 555 timer (IC1)

1 BC548 NPN transistor (Q1)

1 1N4004 1A diode (D1)

1 1N914, 1N4148 signal diode (D2)

1 red 5mm LED (LED1)

Miscellaneous

1 Electronic Doorbell PC board

1 SPDT slider switch (S1)

1 momentary PC-mount pushbutton switch (S2)

4 PC stakes

1 40mm 8Ω Mylar cone speaker

